DDR-3000 VFD Wiring

- 1) Toshiba VFD with conduit enclosure
- #12 black stranded wire 6' long
-) 6 pieces of #12 |) 2 pieces of #12 |) 8 fork lugs green stranded wire - 6' long
- 5) Wire markers 6) 4" piece of # 4" piece of #16 wire for jumper

- Procedure: 1) Install a fork lug on one end of each of the 8
- 2) Take the 6 black wires and lable on both ends as follows: L1, L2, L3. T1, T2, T3
- 3) Run all 8 wires (6 Black & 2 Green) from the VFD to the absolent thru the $\frac{3}{4}''$ liquid tight conduit, keeping the spade lug at the VFD.
- 4) Install the wires in the VFD by removing the clear plate and installing the wires to treminals L1, L2, L3, T1, T2, T3 and on the grouding bar.
- 5) If starting from external sorce install a jumper (#14 or #16 wire) between CC and F



